

Fig. 4. Timing of control lines

put of IC3 is latched by IC5a when the key is released. When a difference in the two digits is detected the Q output of IC5(a) will go high, causing a low to be latched into IC5(b). The low at IC5(b)'s output will then reset the address counter for the RAM and so the VALID output will be prevented from going high. The output of IC5(b) must be SET high again which is done by pressing the '*' key - this should make it more difficult for anybody to 'stumble' across the correct code.

Fig 4 shows the sequence of data on the control lines when a key is pressed. IC4(b), C3 and R4 act as a monostable and the short pulse produced by IC4(b) is used for strobing the SELECT line of the RAM, in programming mode, to cause the data on the bus to be latched. As the strobe pulse occurs on the falling edge of the SID output of IC2 the data is sure to be stable on the bus. The rising edge of this pulse, after inversion by IC4(e), increments the RAM address on IC9, ready for the next number to be stored. During validation the C5

line of the RAM does not need to be strobed and so the line is held permanently low when the PROG line goes high, via IC4(f) and IC7a. IC5(a) is used to latch the output of the comparator just as the key is released, this prevents an incorrect reset pulse being produced by IC3 when the RAM address is incremented and the input from the user is being waited for.

The four bit output on the user port can now be decoded as required. If ten separate control lines are required (for example 0-9) then this can be done simply by connecting a 74LS164 on the output bus and using the VALID line to control its ENABLE input. It is important to remember that the '0' button actually produces the number ten at the output (1010 in binary), not a zero. The display suggested in figures (1) and (2) is provided using the circuit in Fig 5), though because of the point just mentioned the output will not be meaningful when zero is entered, nor '*' and '#'.

Components

Resistors	R1	3.3K Ω
	R2	330K Ω
	R3	270K Ω
	R4	1M Ω
	R5	1M Ω
	RSIL1	10 SIL resistor array
Capacitors	C1	0.1 μ F
	C2	0.1 μ F
	C3	0.1 μ F
	C4	100 μ F Electrolytic
	C5	10 μ F Electrolytic
	C6	0.1 μ F
	C7	10 μ F Electrolytic
	C8	0.1 μ F

Semiconductors	IC1	4063 - 4-bit comparator
	IC2	MV8870-1 - DTMF decoder
	IC3	4063 - 4-bit comparator
	IC4	74LS14 - Hex inverter
	IC5	74LS74 - Dual D-type flip-flop
	IC6	74LS244 - Tri-state buffer
	IC7	74LS08 - Quad AND
	IC8	2114 - Static RAM
	IC9	74LS93 - 4-bit counter
	IC10	74LS93 - 4-bit counter
	IC11	7805 - +5V regulator

Miscellaneous

- 3.579545MHz NTSC Crystal
- Cheap microphone or magnetic telephone pick-up
- 43 strips x 80 holes stripboard
- Mains power adaptor delivering from 7V to 17V DC at at least 150mA

Construction

The circuit can be built on a piece of Veroboard of 43 strips width by 80 holes. Power supply decoupling capacitors should be provided for each chip of 0.1 μ F. The power supply into the regulator can be between 7V and 17VDC and if the answering machine used with the circuit has an external transformer, as most do, this should be able to power both this board and the answering machine (the board requires around 150mA current). The DTMF decoder is the only part not widely available. This was bought through ESD Electronic Services - Tel. (0279) 626777, part

 


Fig. 5. Display decoding.